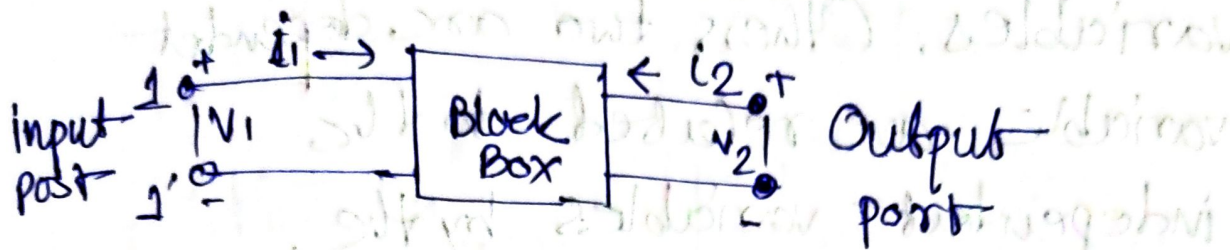


Transistor as a two-port device & Hybrid model.



After the establishment of Q-point, suitable DC values of voltages & currents, alternating current or voltage are applied to a pair of input terminal of the transistor amplifier. This linear performance of the amplifier can be studied analytically by regarding the transistor in any one of its modes as a black box having a pair of input & output terminals. So, there are four variables input current i_1 , input voltage V_1 , output current i_2 , output voltage V_2 .

The input current i_1 & the output voltage v_2 are taken as independent variables. Others two are dependent variables, are related to the independent variables by the following eqⁿ.

o) h_{22}

$$v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

define

col

o) hence, $h_{11} = \left(\frac{v_1}{i_1} \right)_{v_2=0}$ = input impedance

with the output port short-circuited for AC

o) $h_{12} = \left(\frac{v_1}{v_2} \right)_{i_1=0}$ = reverse voltage amplification factor


with the input port open-circuited for AC

o) $h_{21} = \left(\frac{i_2}{i_1} \right)_{v_2=0}$ = current gain with

the output short-circuited for AC


$h_{22} = \left(\frac{i_2}{V_2} \right)_{i_1=0}$ = output admittance
 with the input port open-circuited.

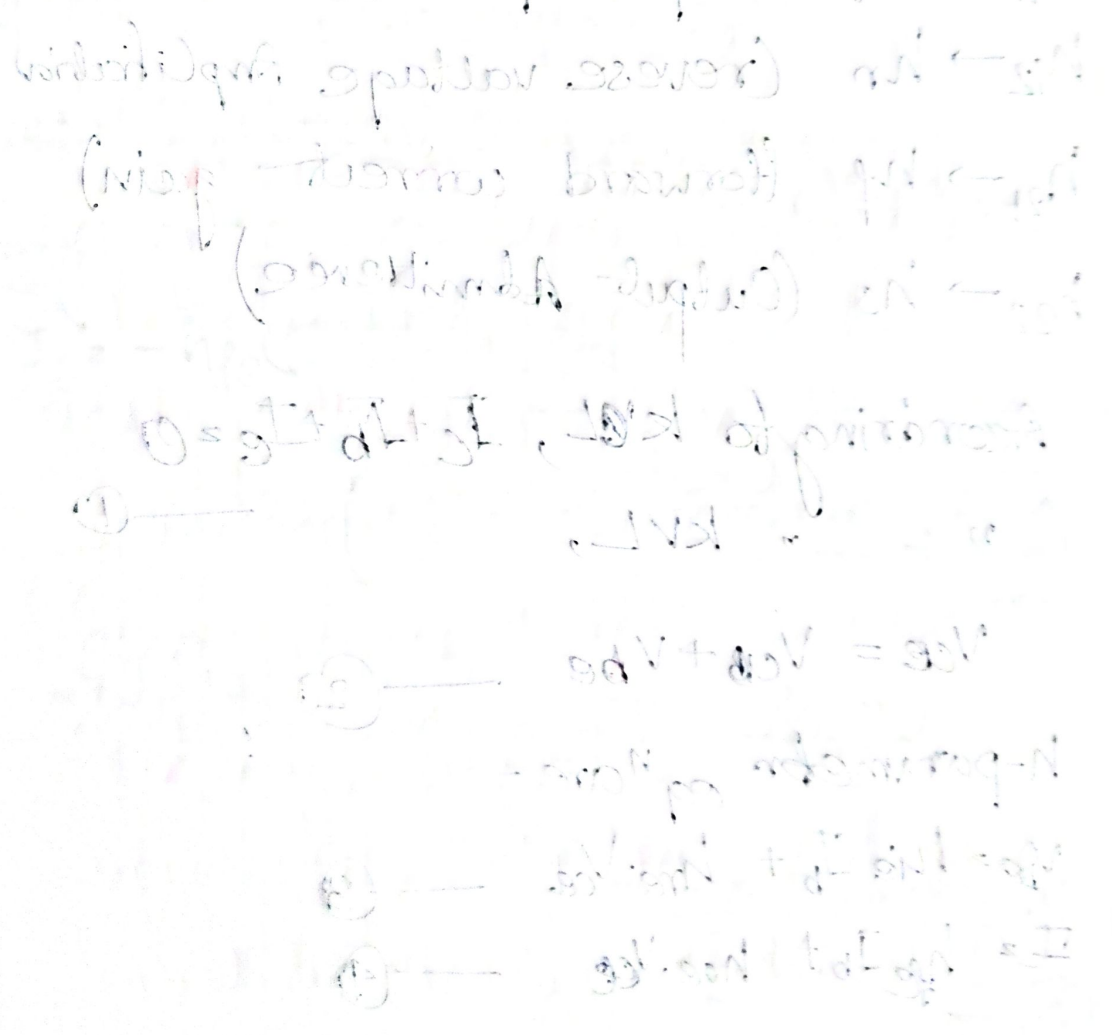Since, h_{11} , h_{22} , h_{12} & h_{21} have different dimensional parameters, they are called hybrid parameters.



wort
 edat
 det
 A
 ionic
 error
 post
 super
 camp
 of the
 cross
 in an
 direct
 direct
 super
 with
 AC

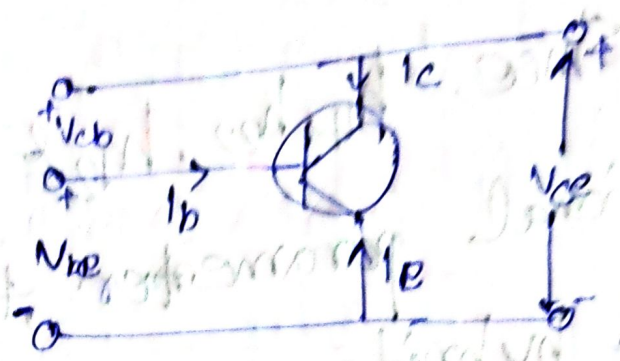Conversion formulas for h-parameters of three transistor modes:



- $h_{11} \rightarrow h_i$ (input impedance)
- $h_{12} \rightarrow h_{re}$ (reverse voltage Amplification)
- $h_{21} \rightarrow h_{fe}$ (forward current gain)
- $h_{22} \rightarrow h_{oe}$ (Output Admittance)

According to KCL, $I_c + I_b + I_e = 0$ — (1)
 " " " KVL,

$V_{ce} = V_{cb} + V_{be}$ — (2)

h-parameter eqⁿ are -
 $V_{be} = h_{ie} I_b + h_{re} V_{ce}$ — (3)

$I_c = h_{fe} I_b + h_{oe} V_{ce}$ — (4)

For Subst
 eq. (2) in

$V_{be} =$
 $V_{be} =$
 V_{be}

Subst
 from

$I_c =$

$I_c =$

\rightarrow

h

Substituting for I_B from eq(1) & V_{CE} from eq(2) in eq(3)

$$V_{BE} = h_{ie}(-I_C - I_E) + h_{re}(V_{CB} + V_{BE})$$

$$V_{BE}(1 - h_{re}) = h_{re}V_{CB} - (I_C + I_E)h_{ie}$$

$$V_{BE} = \frac{h_{re}V_{CB} - (I_C + I_E)h_{ie}}{(1 - h_{re})} \quad \text{--- (5)}$$

Substituting for I_B from eq(1) & V_{CE} from eq(2) in eq(3)

$$I_C = h_{fe}(-I_C - I_E) + h_{oe}(V_{CB} + V_{BE})$$

$$I_C = -h_{fe}(I_C + I_E) + h_{oe}$$

$$h_{oe} \left(\frac{h_{re}V_{CB} - (I_C + I_E)h_{ie}}{(1 - h_{re})} + V_{CB} \right)$$

$$\Rightarrow I_C \left(1 + h_{fe} + \frac{h_{oe}h_{ie}}{1 - h_{re}} \right) = -h_{fe}I_E$$

$$+ h_{oe} \left(\frac{h_{re}V_{CB} - I_C h_{ie}}{(1 - h_{re})} + V_{CB} \right) \quad \text{--- (6)}$$

$$h_{re} \ll 1 \quad \& \quad h_{oe} \cdot h_{ie} \ll 1$$

$$I_c(1+h_{fe}) = h_{fe}I_e + h_{oe}V_{cb}$$

$$I_c = \frac{h_{fe}I_c}{1+h_{fe}} + \frac{h_{oe}}{1+h_{fe}}V_{cb} \quad \text{--- (6)}$$

h-parameter eqⁿ for Cb mode

$$I_c = h_{fb}I_e + V_{cb}h_{ob} \quad \text{--- (7)}$$

compare 6 & 7

$$h_{fb} = \frac{h_{fe}}{1+h_{fe}} \quad h_{ob} = \frac{h_{oe}}{1+h_{fe}}$$

$$\left(\frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain} = \left(\frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain}$$

$$\text{gain} + \left(\frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain} = \text{gain}$$

$$\left(\frac{h_{fe}}{1+h_{fe}} + \frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain}$$

$$\text{gain} = \left(\frac{h_{fe}}{1+h_{fe}} + \frac{h_{fe}}{1+h_{fe}} \right) \cdot I_e$$

$$\left(\frac{h_{fe}}{1+h_{fe}} + \frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain}$$

(8)

$$\text{gain} \gg \left(\frac{h_{fe}}{1+h_{fe}} + \frac{h_{fe}}{1+h_{fe}} \right) \cdot \text{gain}$$